

# Serial Adder with Library of Parameterized Modules as Building Blocks

Mun'im Zabidi

## Abstract

This documents gives the basic steps in implementing a serial adder in Altera Quartus.

<sup>1</sup> Department of Electronic and Computer Engineering, School of Electrical Engineering, Faculty of Engineering

\*Corresponding author: munim@utm.my

## 1. Overview

A digital system is first defined with the specification of the top level component (entity) and the algorithm to be performed. From the specifications, the appropriate port interface is defined.

 


Figure 1. Serial Adder entity.

### Inputs

- **A:** First  $n$ -bit Operand (Addend)
- **B:** Second  $n$ -bit Operand (Augend)
- **st:** Start signal which initiates the addition operation
- **rst:** Reset signal which puts the controller into the initial state

### Outputs

- **S:** The  $(n+1)$ -bit sum with carry ( $S = A + B$ )
- **done:** Active when the operation is complete

The algorithm is as follows:

```
Load A, Load B
c = 0, k = 0
while (k < n)
  {c, S[k]} = A[k] + B[k] + c
  k = k + 1
endwhile
done = 1
```

where  $n$  is the number of bits,  $c$  is the carry-in bit and  $k$  is a counter variable which goes from 0 to  $n - 1$ . Variables on the left-hand side of the equations are normally need to be stored in registers, hence, we infer that two  $n$ -bit registers  $A$  and  $B$ , and a 1-bit carry register,  $c$  are needed. An  $(n + 1)$ -bit register  $S$  stores the sum. Since the addition is performed in a serial fashion, a 1-bit adder is needed.

In practical designs, a down counter is preferred over an up counter because detecting a final value of 0 is trivial. Therefore, the pseudo-code is modified as follows:

```
Load A, Load B
c = 0, k = n
while (k > 0)
  {c, S[n-k]} = A[n-k] + B[n-k] + c
  k = k - 1
endwhile
done = 1
```

## 2. First-Cut Circuit

A serial adder consists of three  $n$ -bit shift registers, a full-adder and a D flip-flop. Two parallel-in-serial-out (PISO) shift registers holds the numbers ( $A$  and  $B$ ) to be added, while a serial-in-parallel-out (SISO) register holds the sum ( $S$ ). The full-adder performs the addition operation on the values stored in the input shift registers and the carry flip-flop in  $n$  clock cycles. A "first-cut" block diagram of a serial adder is shown in Figure 2.

During each clock cycle, the current least significant bits of the  $A$  and  $B$  registers,  $a_0$  and  $b_0$ , with the current carry-in,  $c_i$  are summed by the full-adder. This produces sum bit  $s_i$  and the carryout bit  $c_{i+1}$ . On the next clock edge,  $s_i$  are shifted into the result register  $S$ . At the same time,  $c_{i+1}$  is stored into the DFF, to prepare for the next set of bits. The

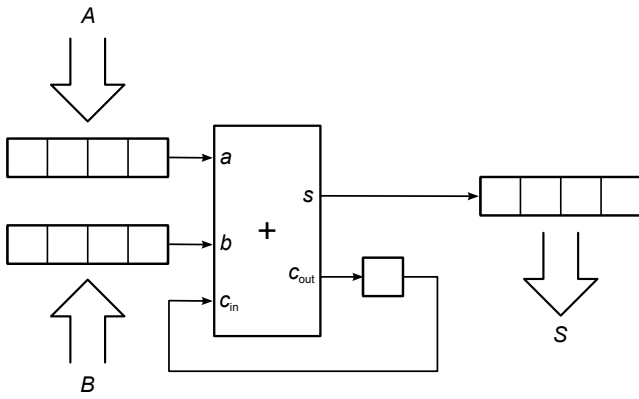


Figure 2. Overview of the serial adder circuit.

Table 1. Sequence of 4-bit serial adder operation performing  $1011 + 0011 + 0 \rightarrow 01110$ .

A	B	$c_i$	$c_{i+1}$	$s_i$	S
1011	0011	0	1	0	----
-101	-001	1	1	1	0----
--10	--00	1	0	1	10--
---1	---0	0	0	1	110-
----	----	0	-	-	1110

sequence of the operation of a 4-bit serial adder is illustrated in Table 1.

The value at the D flip-flop,  $c_i$ , is the carry-out from the whole addition. This bit can be combined with S to form the 5-bit result.

The serial adder completes the addition process in 4 clock pulses. Shifting of the registers must be stopped after completion. Otherwise, the computed result will be shifted out and disappear.

### 3. Datapath Overview

Figure 3 shows the top level circuit diagram for a 4-bit serial adder based in on the first-cut circuit. A 2-bit counter and muxes at the DFF input are now part of the datapath. The signals needed for controlling this DPU are:

- **en\_ld**: Load the register/counter
- **en\_sh**: Enable shift register operation
- **en\_ct**: Enable counter operation. Later we found out we do not need this signal.

Here's how it operates:

- In idle state, the FSM waits for *st* (start) signal while continuously loading A, B registers, clearing D and loading counter K with 3.
- When start signal is received, repeat the following 4 times:
  - Shift registers A, B, S and flip-flop D
  - Decrement downcounter K

- After the bits have been shifted 4 times (signaled by Zero signal from downcounter), stop shifting and output the *done* signal. The 5-bit sum is now stable and correct.

The high-level ASM as shown in Fig. 4 describes the tasks done by the circuit.

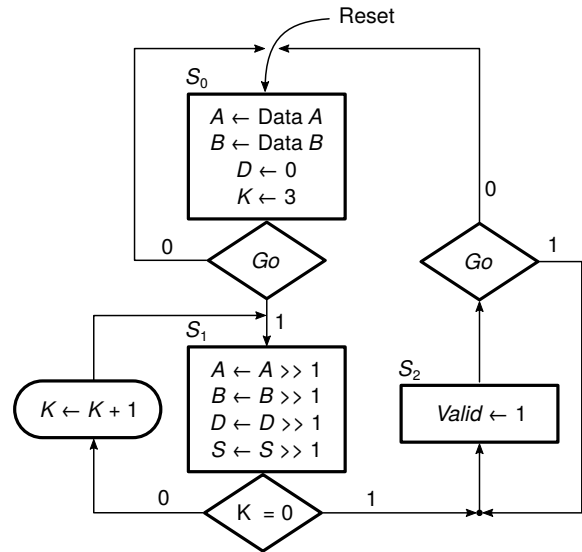


Figure 4. High-level ASM for serial adder.

## 4. Building Blocks

After the top-down design stage comes the bottom-up implementation stage. The modules to be built are:

- Full adder
- DFF with enable and clear
- PIPO register
- SIPO register
- Downcounter

### 4.1 Full adder

The full adder is constructed by combining two half-adders and an OR gate (Fig. 5 and Fig. 6).

 


Figure 5. Half adder component.

 


Figure 6. Full adder component.

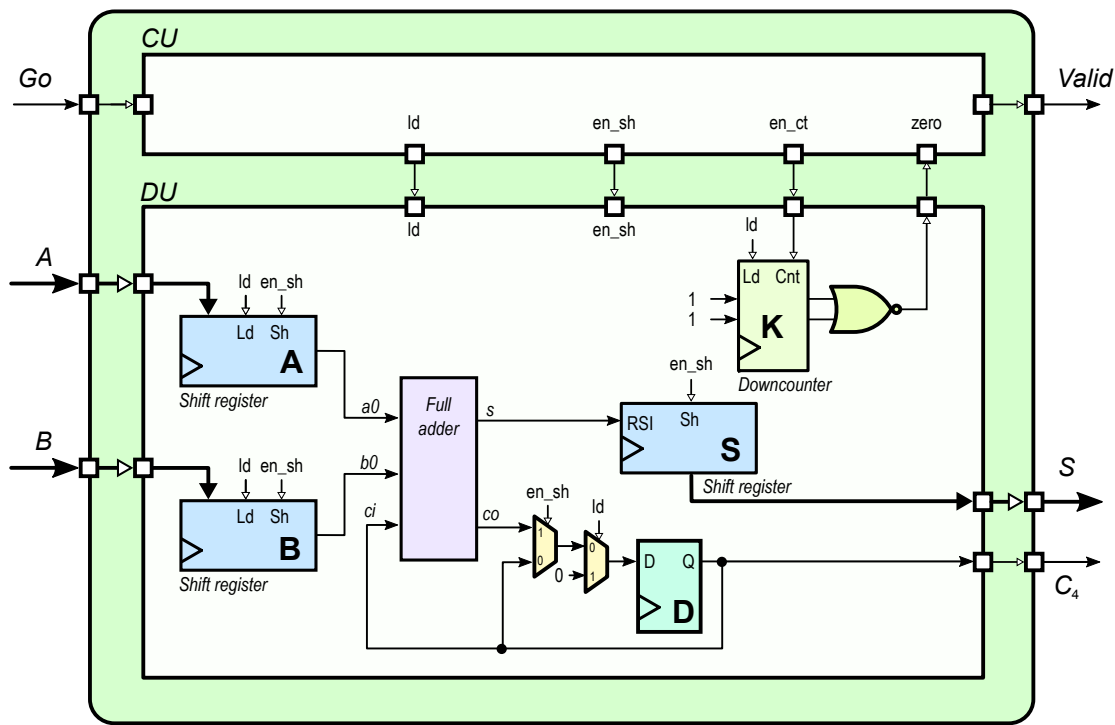


Figure 3. Serial adder datapath.

#### 4.2 DFF with enable and clear

A basic DFF loads a new value every time a clock pulse arrives. For this serial adder, a custom DFF circuit is required because we want to stop loading when the operation is completed. The *D flip-flop with enable and clear* (DFEFC) shown in Fig. 7 has two additional controls:

- **load:** to load a new value into the flip-flop
- **clear:** to clear the flip-flop

 


Figure 7. D flip-flop with enable and clear.

In the serial adder datapath architecture, the **ld** signal initializes all registers to prepare for adding a new set of numbers. Connecting the **ld** signal to the **clear** input of the DFF modules prepares the DFF adding the first bit pair.

#### 4.3 SIPO Shift Register

The serial-in-parallel-out (SIPO) shift register receives a sum bit from the full adder, one bit at a time. Data is inserted serially through the right shift input.

In Quartus, first choose the **lpm\_shiftreg** megafunction. On the first pop-up screen (Fig. 8), choose the following settings:

- Output bus width: 4

- Shift direction: *right*
- *Data output*
- *Clock enable* input
- *Serial shift data input*

Then click Finish.

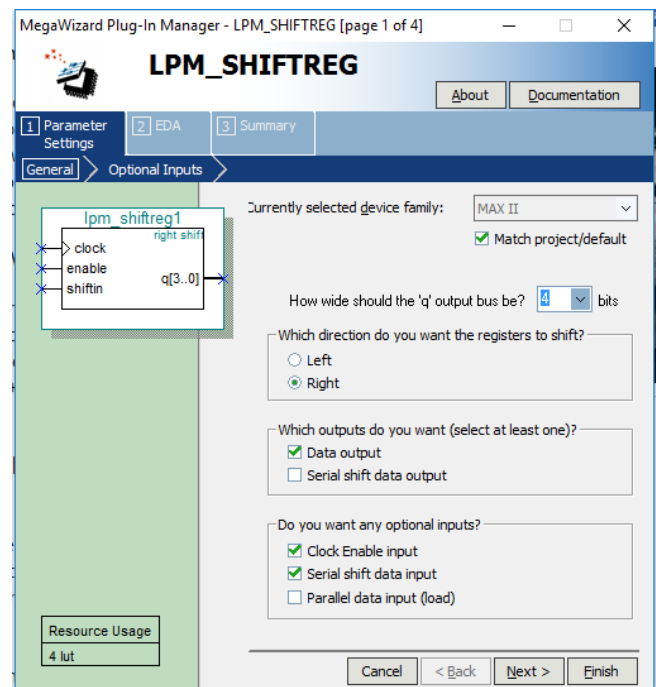


Figure 8. Setting the parameters SIPO shift register.

#### 4.4 PISO Shift Register

Two parallel-in-serial-output (PISO) registers are required. Repeat the following procedure in Quartus twice.

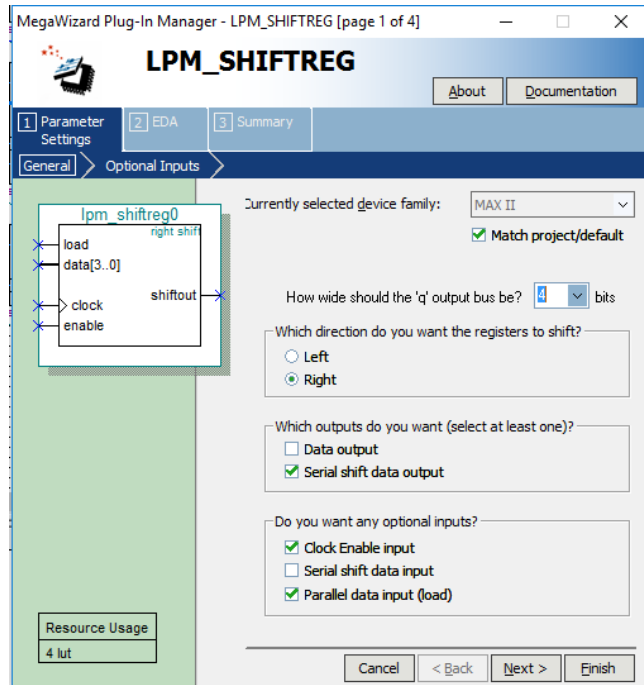


Figure 9. Setting the parameters for a PISO shift register.

First choose the **lpm\_shiftreg** megafunction. On the first pop-up screen (Fig. 9), choose the following settings:

- Output bus width: 4
- Shift direction: *right*
- *Data output* (Not strictly needed for this project but choosing it allows us to see the internal operation of the SIPO.)
- *Serial shift data output*
- *Clock enable input*
- *Parallel data input (load)*

Then click Finish.

#### 4.5 Loop control counter

This counter controls how many times a task is repeated. The counter is initialized with the number of loops required minus 1 and counts down to 0. To repeat a task 3 times, load the counter with 3. Each time a task is performed, the counter is decremented by 1. At zero, a NOR gate sends a *zero* signal to the controller.

In Quartus, first choose the **lpm\_counter** megafunction. On the first pop-up screen (Fig. 10), choose the following settings:

- Output bus width: 2
- Count direction: *down only*

Click Next to get the second pop-up screen. On the second pop-up screen, just click Next to skip the options and get the third pop-up screen.

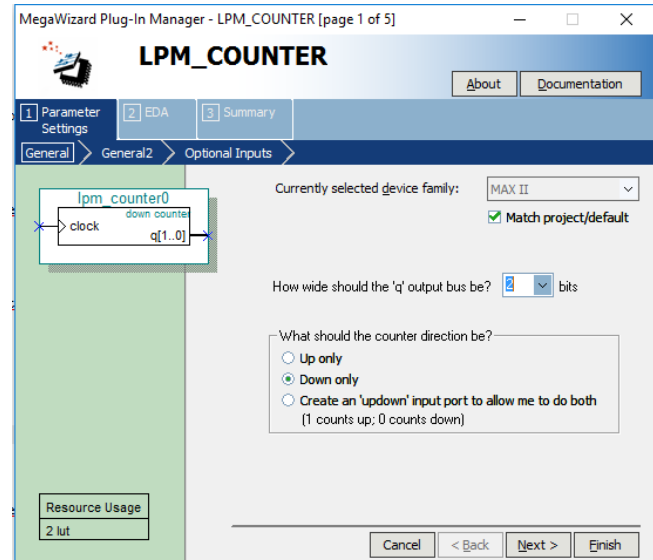


Figure 10. Setting the parameters for a simple down counter.

On the third pop-up screen (Fig. 11), in the synchronous inputs box, select:

- *Set*
- *Set to all 1's*

This last option creates the **sset** input. Whenever this input is high, the counter is loaded with 3. When this input is low, the counter immediately counts down.

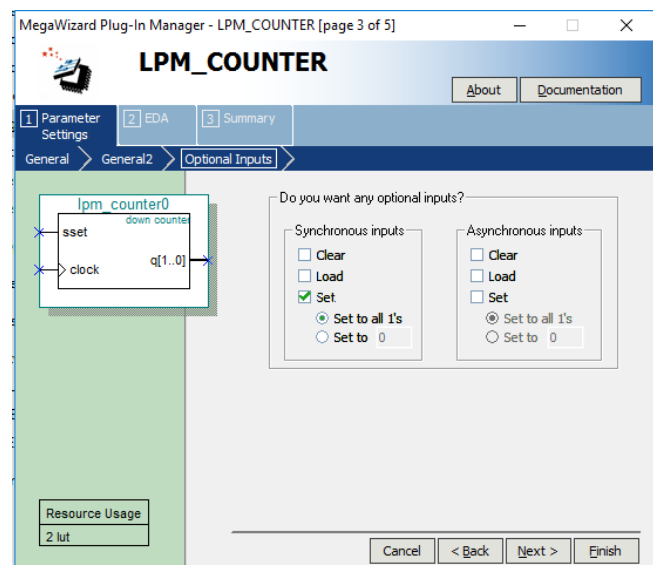


Figure 11. Choosing a pre-load value of 3.

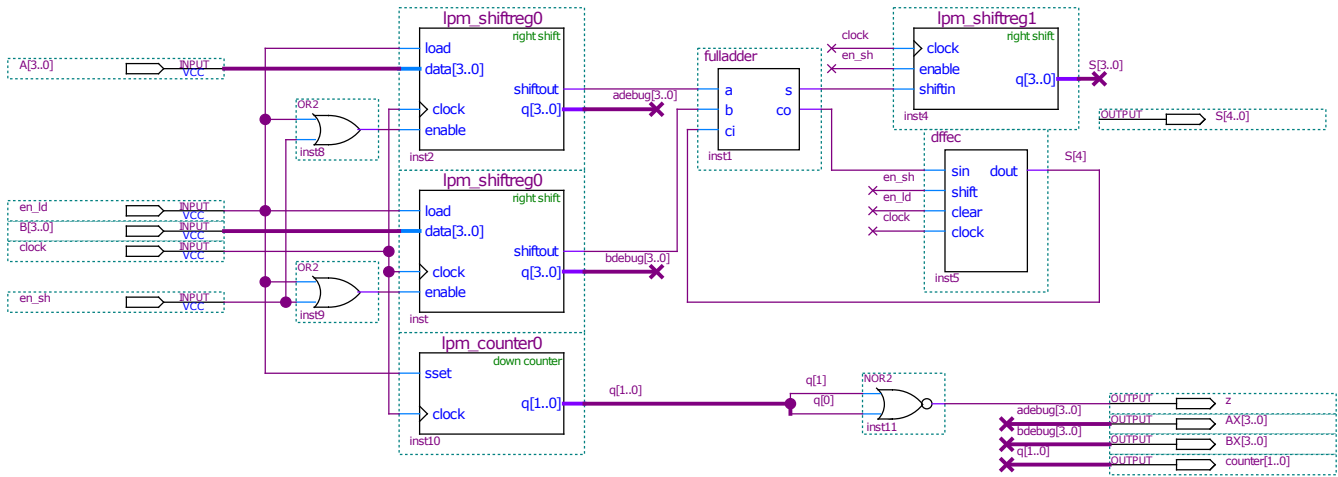


Figure 12. Serial adder datapath unit.

### 5. Datapath Unit Integration

When all building blocks are completed, they are integrated to form the datapath circuit as shown in Fig. 12. The datapath is tested by setting the inputs via a waveform editor. Once the datapath design is verified, we are ready to design the controller.

Input port types:

- Clock
- Data inputs A and B directly from an external system.
- Inputs from the control unit: **en\_sh** to enable shifting and adding, and **en\_ld** to initialize all registers.

Output port types:

- **Zero** tells the control unit that counter has reached 0
- Data outputs to an external system.

Two OR gates are added to the enable input of the PISO because to perform shifting, **enable** must be high but to perform loading, both **enable** and **load** inputs must high at the same time.

Outputs AX[3:0], BX[3:0] and counter[1:0] are optional outputs to help us understand what is happening the circuit.

Output ports are two types.

- **Zero** to tell the control unit that counter has reached 0
- Data outputs to an external system.

Simulation of the datapath unit is shown in Fig. 13. On the first clock edge, **en\_ld** is high to initialize all registers ( $A \leftarrow 5, B \leftarrow 13, D \leftarrow 0, K \leftarrow 3$ ). On the four subsequent clock edges, **en\_sh** is high to enable adding and storage of result bits. It is important to disable this signal after four clock edges to freeze the result.

 


Figure 13. Simulation of datapath unit.

### 6. Control Unit

The controller automates the datapath operation. The low-level ASM in Fig. 14 defines the actual status and control signals required for control unit operation.

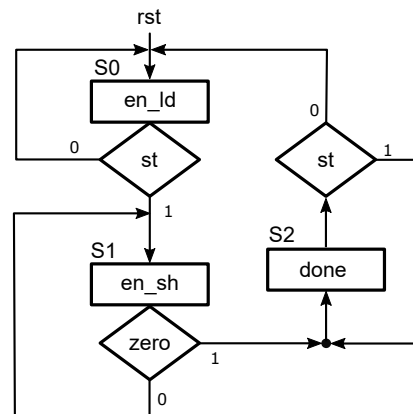


Figure 14. Low-level ASM for serial adder.

The control unit is implemented using the almost-one-hot state assignment. We get the following next state equa-

tions:

$$S0 = \overline{S0} \cdot \overline{S1} \cdot \overline{S2} + S0 \cdot \overline{st} + S2 \cdot \overline{st}$$

$$S1 = S0 \cdot st + S1 \cdot \overline{zero}$$

$$S2 = S1 \cdot zero + S2 \cdot st$$

The output equations are read directly from the ASM chart:

$$en\_ld = S0$$

$$en\_sh = S1$$

$$done = S2$$

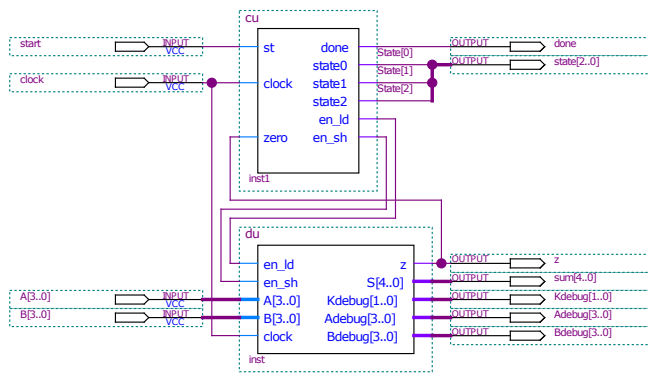


Figure 16. Serial adder top level entity.

The control unit is then combined with the datapath unit in the top level entity circuit in Fig. 16. The simulation of the complete serial adder is shown in Fig. 17.

When using a controller based on the almost one-hot assignment, remember to wait one clock cycle for the flip-flops to transition from 000 (“boot” or initial state) to 001 (state S0).

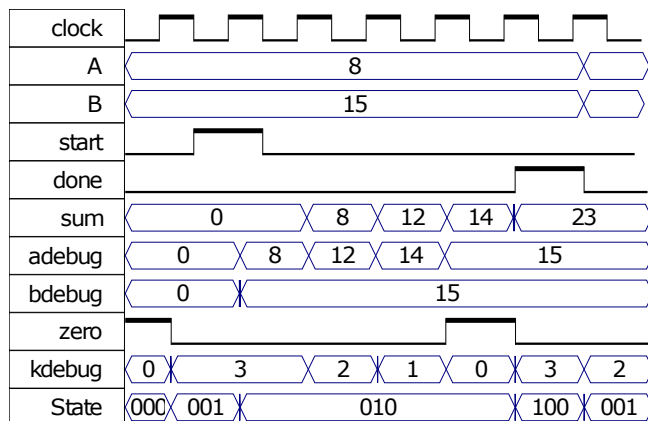


Figure 17. Simulation of serial adder for 8 + 15.

## References

- [1] *Designing State Machines for FPGAs*. Actel Corporation. Sept. 1997.
- [2] Steve Golson. “One-hot state machine design for FPGAs”. In: *Proc. 3<sup>rd</sup> Annual PLD Design Conference & Exhibit*. Vol. 1. 3. 1993.
- [3] David A Huffman. “The synthesis of sequential switching circuits”. In: *Journal of the Franklin Institute* 257.3 (1954).
- [4] Munim Zabidi, Izam Kamisian, and Ismahani Ismail. *The Art of Digital Design*. 2019.
- [5] *Introduction to the Quartus® II Software*. Version 10. Altera. 2010. URL: [https://www.intel.com/content/dam/www/programmable/us/en/pdfs/literature/manual/intro\\_to\\_quartus2.pdf](https://www.intel.com/content/dam/www/programmable/us/en/pdfs/literature/manual/intro_to_quartus2.pdf).
- [6] Stephen Brown and Zvonko Vranesic. *Fundamentals of Digital Logic with Verilog Design*. 3rd ed. McGraw-Hill Education, 2013.

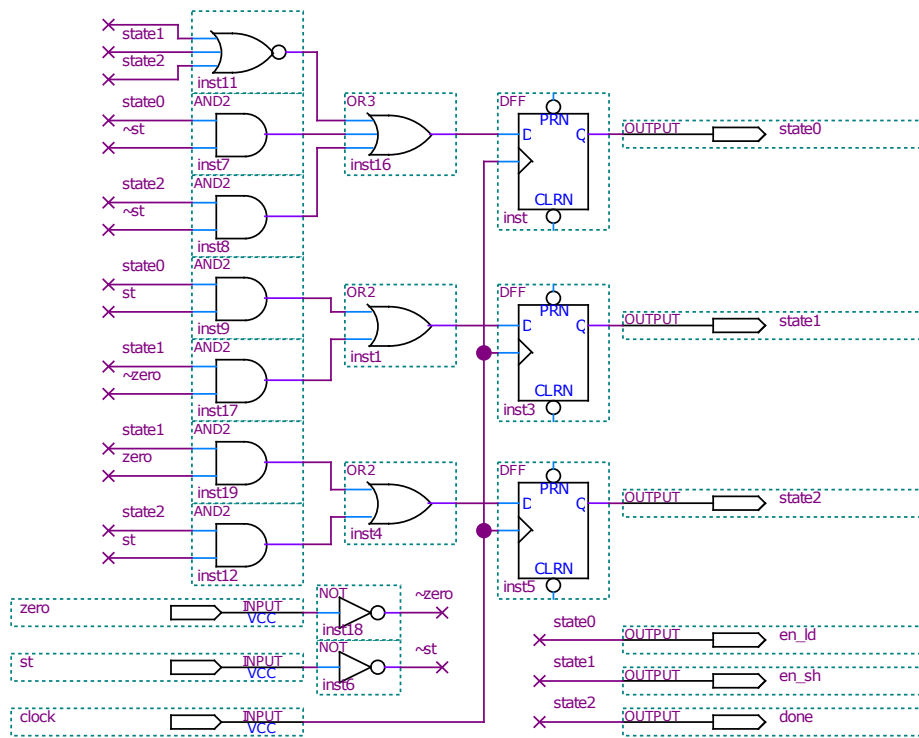


Figure 15. Control unit.