

Faculty <b>FACULTY OF ELECTRICAL ENGINEERING</b>	
Subject : <b>MAKMAL KEJ. ELEKTRIK</b>	Review : <b>4</b>
Subject Code : <b>SKEU 3741</b>	Release Date : <b>Julai 2011</b>
	Last Amendment : <b>Jun 2010</b>
	Prosedure No : <b>PK-UTM-FKE-(O)-08</b>



**FAKULTI KEJURUTERAAN ELEKTRIK  
UNIVERSITI TEKNOLOGI MALAYSIA  
KAMPUS SKUDAI  
JOHOR**

## **SKEU 3741 ELECTROTECHNIC LABORATORY**

### **(Experiment 1)**


# **SERIES AND PARALLEL RESONANCE CIRCUIT CHARACTERISTICS**

<b>Prepared by:</b> <ol style="list-style-type: none"><li>1. PM. Dr. Mohd Wazir B. Mustafa</li><li>2. En. Alias B. Mohd. Yusof</li><li>3. En. Abd. Jaafar B. Shafie</li><li>4. Dr. Saifulnizam B. Abd. Khalid</li><li>5. Zaniah Bt. Muda</li><li>6. Faridah Bt. Hussin</li><li>7. Nur 'Ain Maiza Ismail</li></ol> <b>Signature and Stamp:</b>   <b>Date:</b>	<b>Approved by:</b> Head of Department Name: Assoc. Prof. Dr. Azhar Khairuddin   <b>Signature and Stamp:</b>   <b>Date:</b>
--	--

**I. PRELIMINARY EXERCISE (10 marks)**

**Important Note: You are required to do this exercise BEFORE the lab session.  
Each question carries 5 marks**

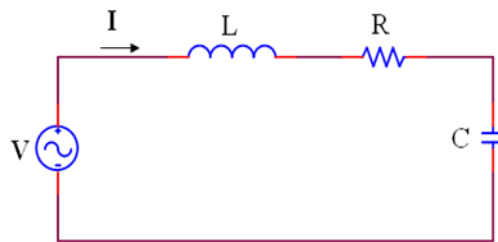
1. For a circuit in Figure 1.0
  - a) Calculate the total impedance (*polar form*), voltage across each element and power factor to fill up Tables 1.1 and 1.3.
  - b) Draw graph Z vs freq and calculate resonance frequency.
  - c) Draw the phasor diagram of the voltage for each element before, during and after resonance. (Use current as reference)



$V = 0.5 \text{ volt}; R = 50\Omega; L = 4 \text{ mH}; C = 0.06 \mu\text{F}$

**Figure 1.0**

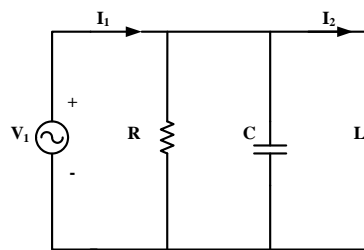2. For a circuit in Figure 2.0,
  - a) Calculate the total admittance (*polar form*), current,  $I_1$  and  $I_2$  and power factor to fill up Table 2.1.
  - b) Draw graph admittance, Y versus frequency.
  - c) Draw the phasor diagram of the currents for each element before, during and after resonance. (Use voltage as reference)



$I_1 = 1 \text{ mA}; R = 10 \text{ k}\Omega; L = 5 \text{ mH}; C = 100 \text{ nF}$

**Figure 2.0**

3. List at least 3 applications of resonance in practice

**Recommended Reference:**

1. Alexander & Sadiku, 'Fundamentals of Electric Circuits', 4<sup>th</sup> edition, McGraw Hill.

## II. EXPERIMENT:

### “Measurement Of Series And Parallel Resonance Characteristics”


#### 1. Aims:

- i. To investigate series and parallel resonance characteristics
- ii. To identify resonant parameters

#### 2. Equipments:

- i. Signal generator
- ii. Volt meter
- iii. Decade inductor (L)
- iv. Decade resistor (R)
- v. Decade capacitor (C)

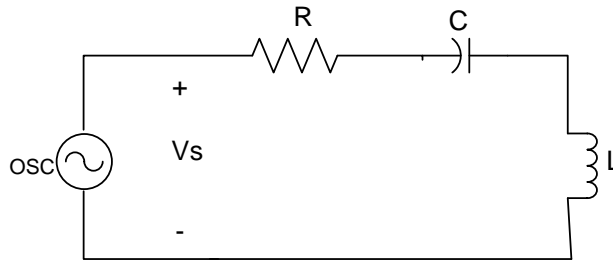3. Figure 1.0 shows a series resonance circuit connection.



R=(refer to Table 1.1 in the Lab Sheet), L=4mH, C=0.06 $\mu$ F

**Figure 1.0**

#### 4. Procedure:

***Precaution:*** Ask your lab instructor to check your circuit connection before you start the experiment.


- i. Connect the circuit as shown in Figure 1.0.
- ii. Set the value of R according to the signal generator model (OSC). You can use either of the signal generator listed below (Table 1.0):

**Table 1.0**

No.	Type/Model of Signal Generator	Set the value of R to :
1.	Jupiter 500	35 $\Omega$
2.	Mei Li	50 $\Omega$
3.	Trio	50 $\Omega$
4.	Levell TG 152DM	0 $\Omega$

- iii. Select the sinusoidal waveform from the signal generator output. Set the amplitude so that the voltage across the source,  $V_S$  is constant at 0.5 volt.
- iv. Fixed the capacitor at  $0.06\mu\text{F}$  and set  $L = 4\text{mH}$ . Varies the value of freq and record the voltage readings  $V_R$ ,  $V_L$  and  $V_C$  as in the Table 1.2. For each value of freq, the source has to be adjusted so that the voltage of the source,  $V_S$  is fixed at 0.5 volt.
- v. Now, fixed the freq at 10 kHz and maintaining  $L = 4\text{mH}$ . Varies the value of capacitor and record the voltage readings  $V_R$ ,  $V_L$  and  $V_C$  as in the Table 1.4. For each value of capacitance, the source has to be adjusted so that the voltage of the source,  $V_S$  is fixed at 0.5 volt.

5. **Figure 2.0 shows a parallel resonance circuit connection.**

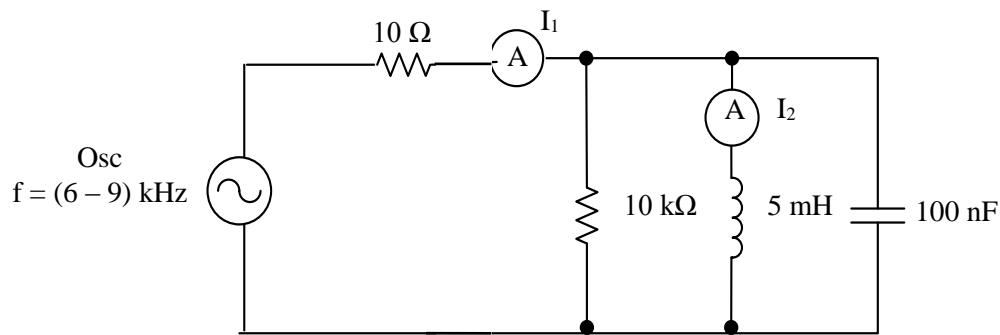

**Figure 2.0**

6. **Procedure:**

**Precaution:** Ask your lab instructor to check your circuit connection before you start the experiment

- i. Connect the circuit as shown in Figure 2.0.
- ii. Select the sinusoidal waveform from the signal generator output. Set the amplitude so that the ammeter  $I_1$  is constant at 1mA. Record the reading of ammeter  $I_2$  for the frequencies range between 6 kHz to 9 kHz as in Table 2.2.